

Names: Kyle Thompson, Konnor Kivimagi

Section: 4

Lab Time: Wednesday 11am – 1:50pm


TAs: Raufer Khan and Yang Tian



## Lab 7: Design Lab - Active crossover network

### Tweeter

The high pass filter or tweeter was designed using the third equation in the figure below. This was used to find a first-order high pass circuit with a cutoff frequency of 6000Hz and a capacitor value of 1 nano-farad to create an input resistance of greater than 10000Ω. Then two of these first-order high pass filters were cascaded together to make a second-order high pass with a cutoff frequency of 6000Hz as shown in the LtSpice figure below.

### High Pass Second Order Filters

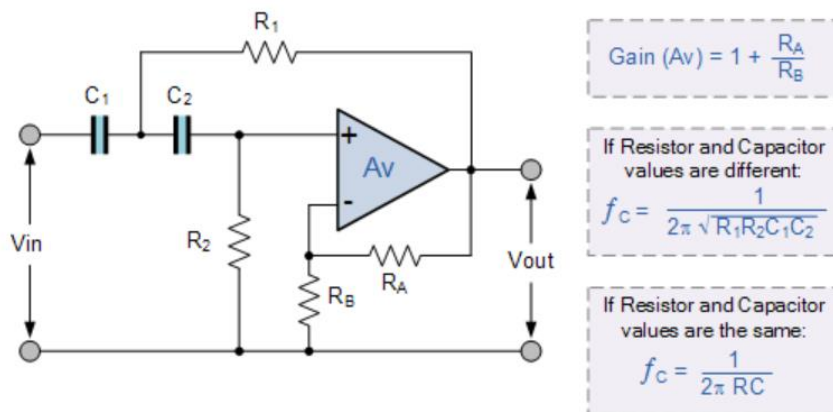


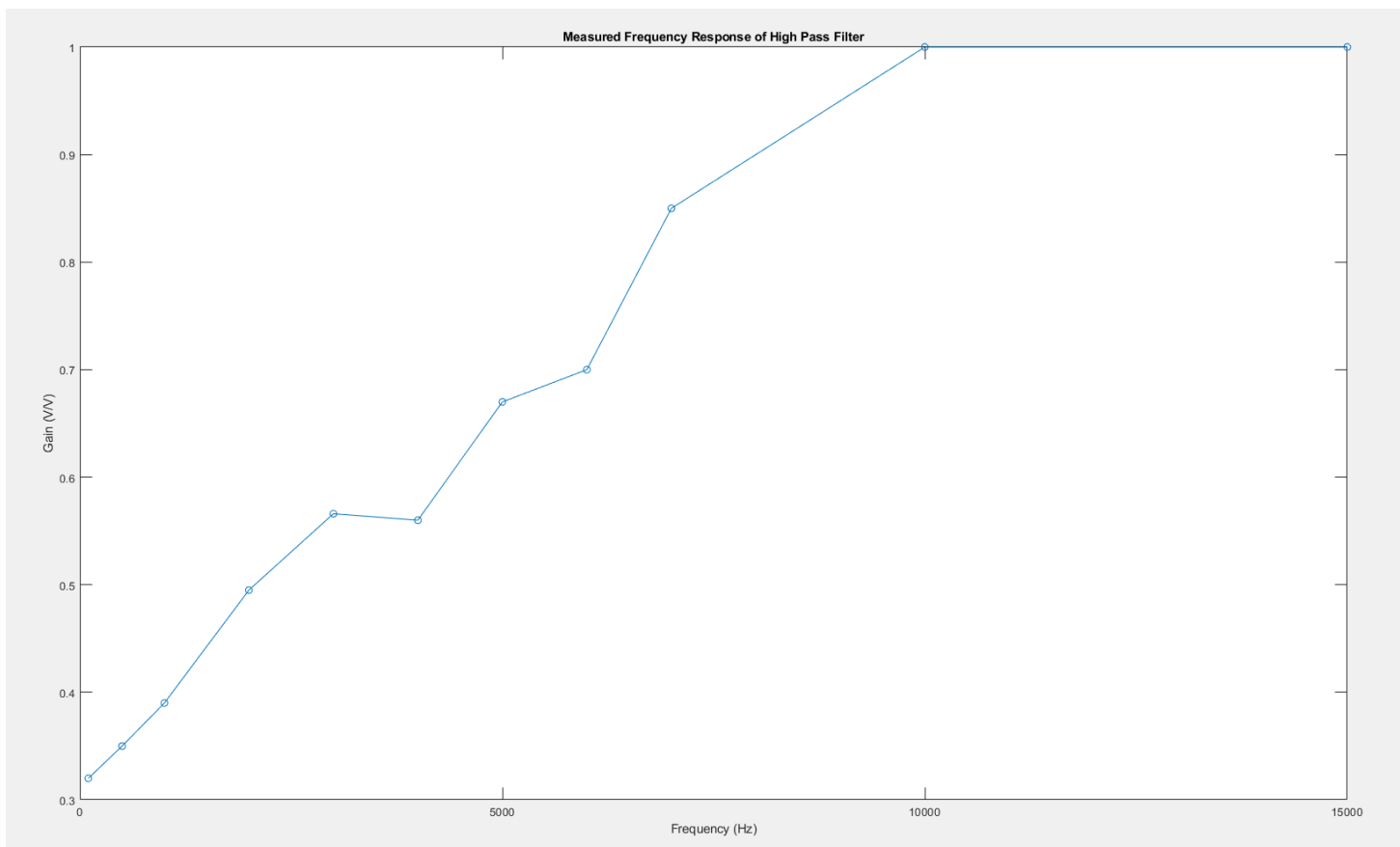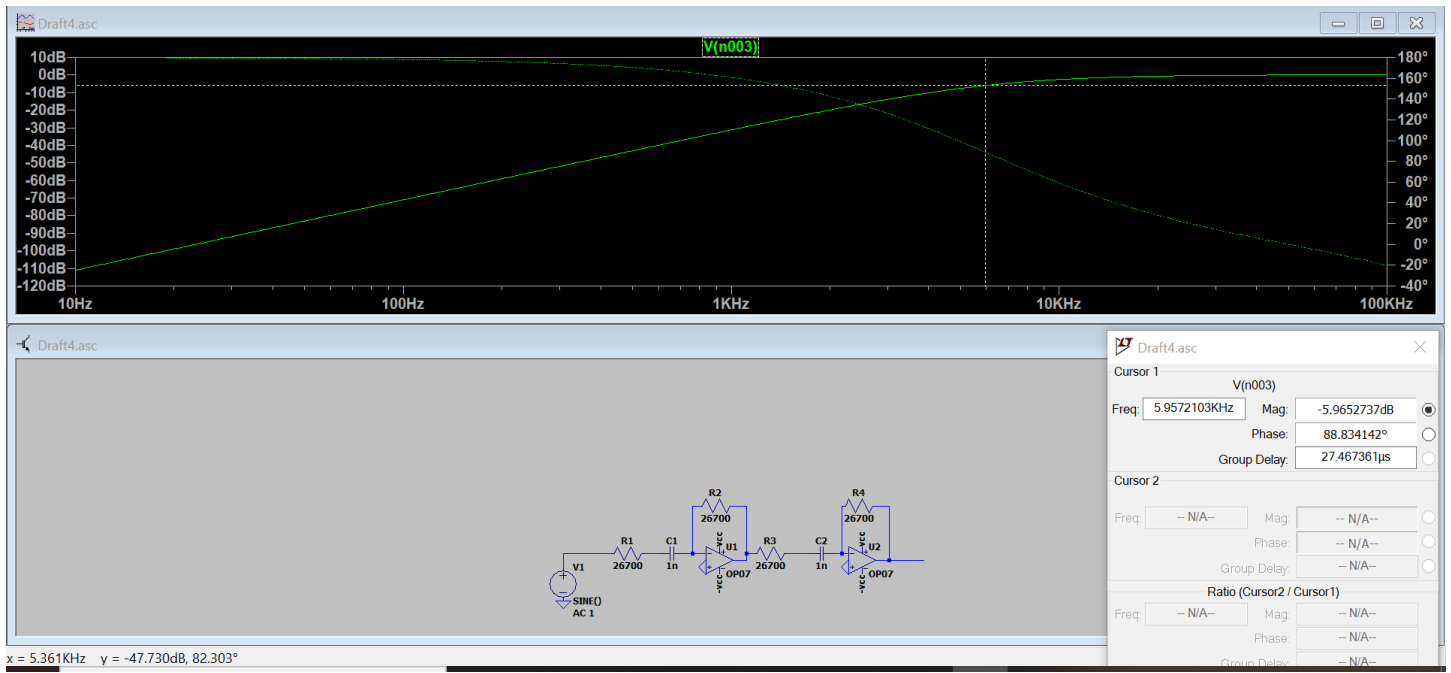

## Woofer

The low-pass filter or woofer was designed using the image and equations shown below. It was designed with an input resistance of  $10000\Omega$  and the ability to change its gain between 1 and 5. The gain was changed by replacing resistor  $R_A$  with a potentiometer.

### Second Order Low Pass Filter

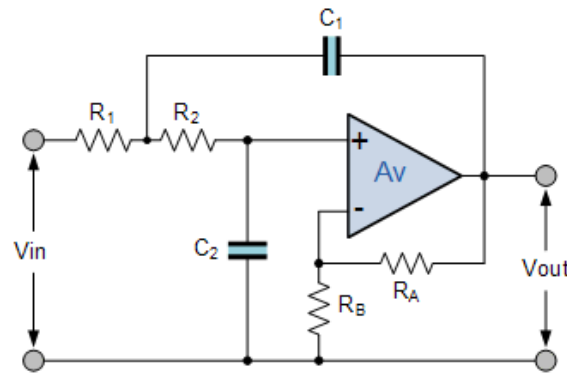


$$\text{Gain } (A_v) = 1 + \frac{R_A}{R_B}$$

If Resistor and Capacitor values are different:


$$f_c = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$



If Resistor and Capacitor values are the same:

$$f_c = \frac{1}{2\pi RC}$$

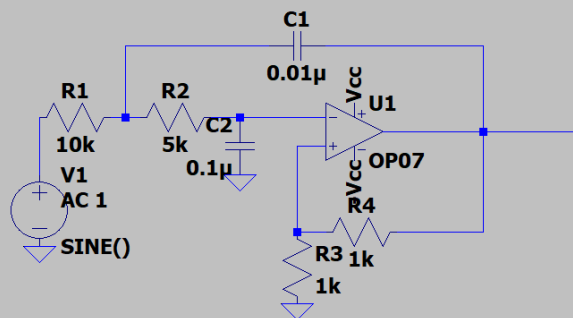

.ac dec 100 10 1000

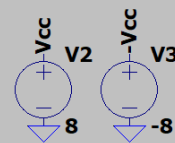


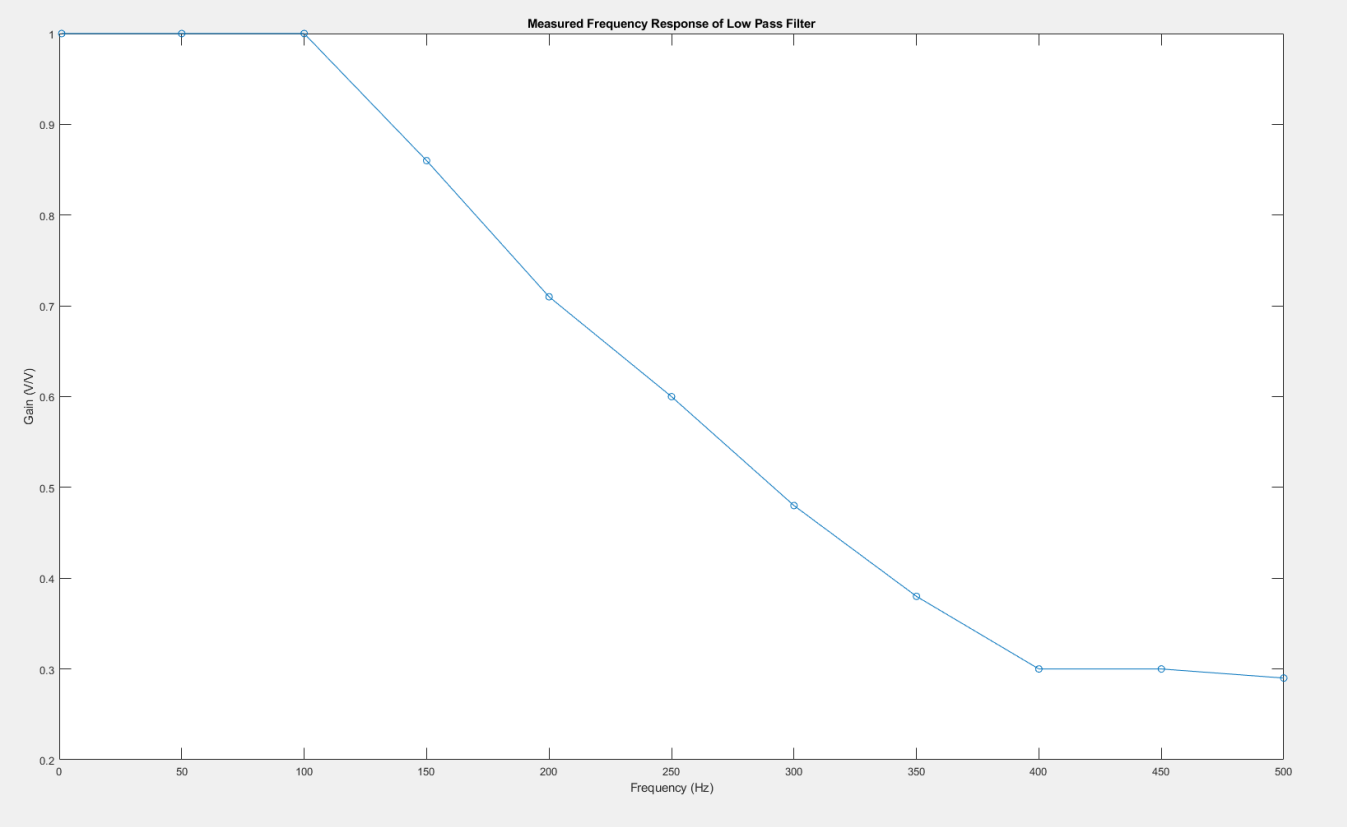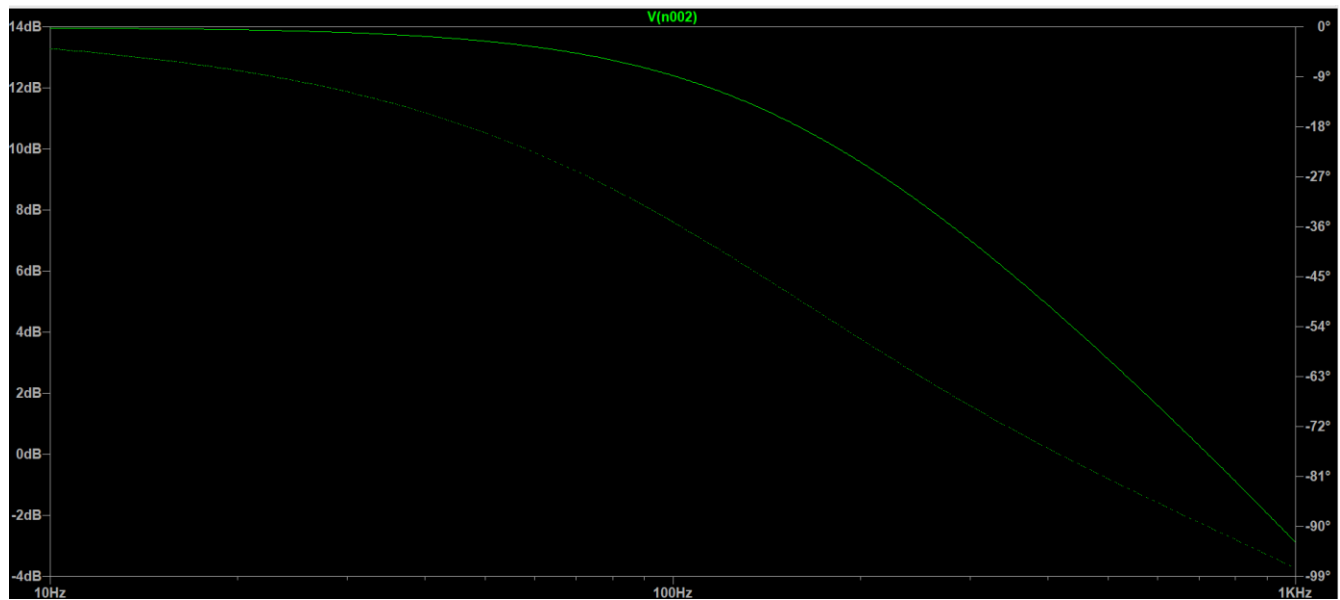


## Squawker



The band pass filter or squawker was designed using the equations and layout pictured in the picture below. The resistor values were chosen to be 150kΩ and had to be equal to obtain a gain of 1. The capacitor values were calculated based on these resistor values.

### Inverting Band Pass Filter Circuit

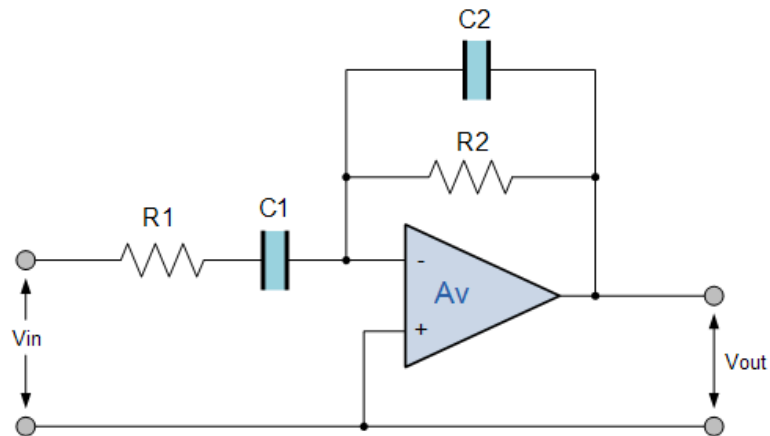
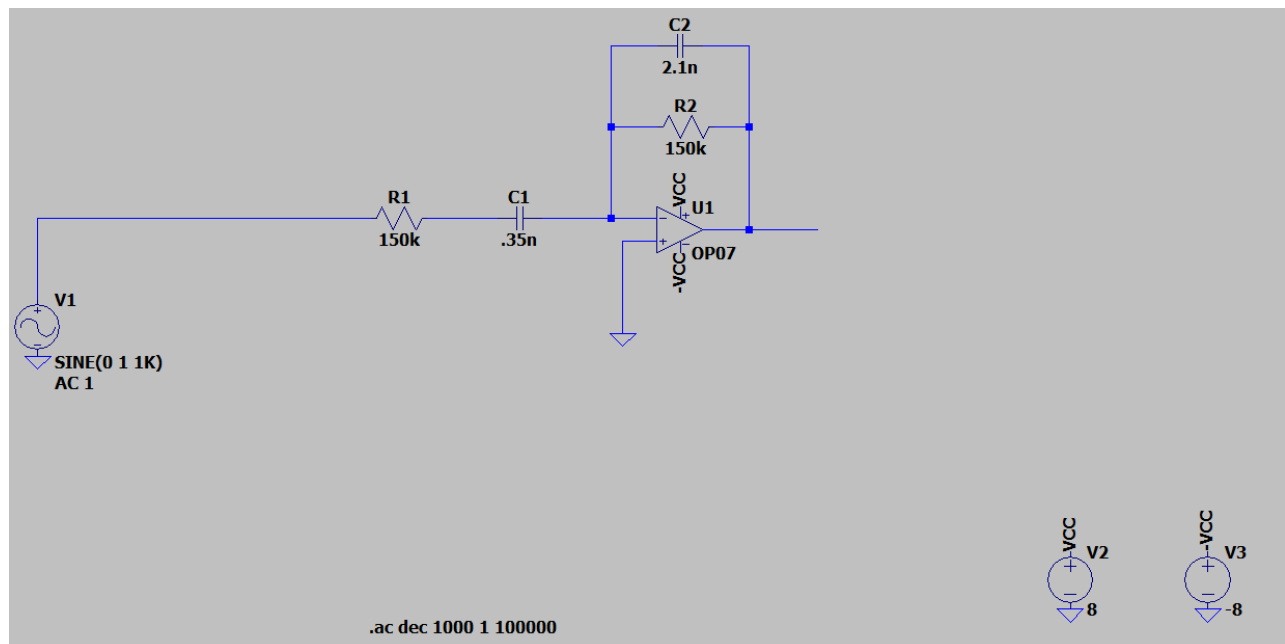
$$\text{Voltage Gain} = -\frac{R_2}{R_1}, \quad f_{c_1} = \frac{1}{2\pi R_1 C_1}, \quad f_{c_2} = \frac{1}{2\pi R_2 C_2}$$



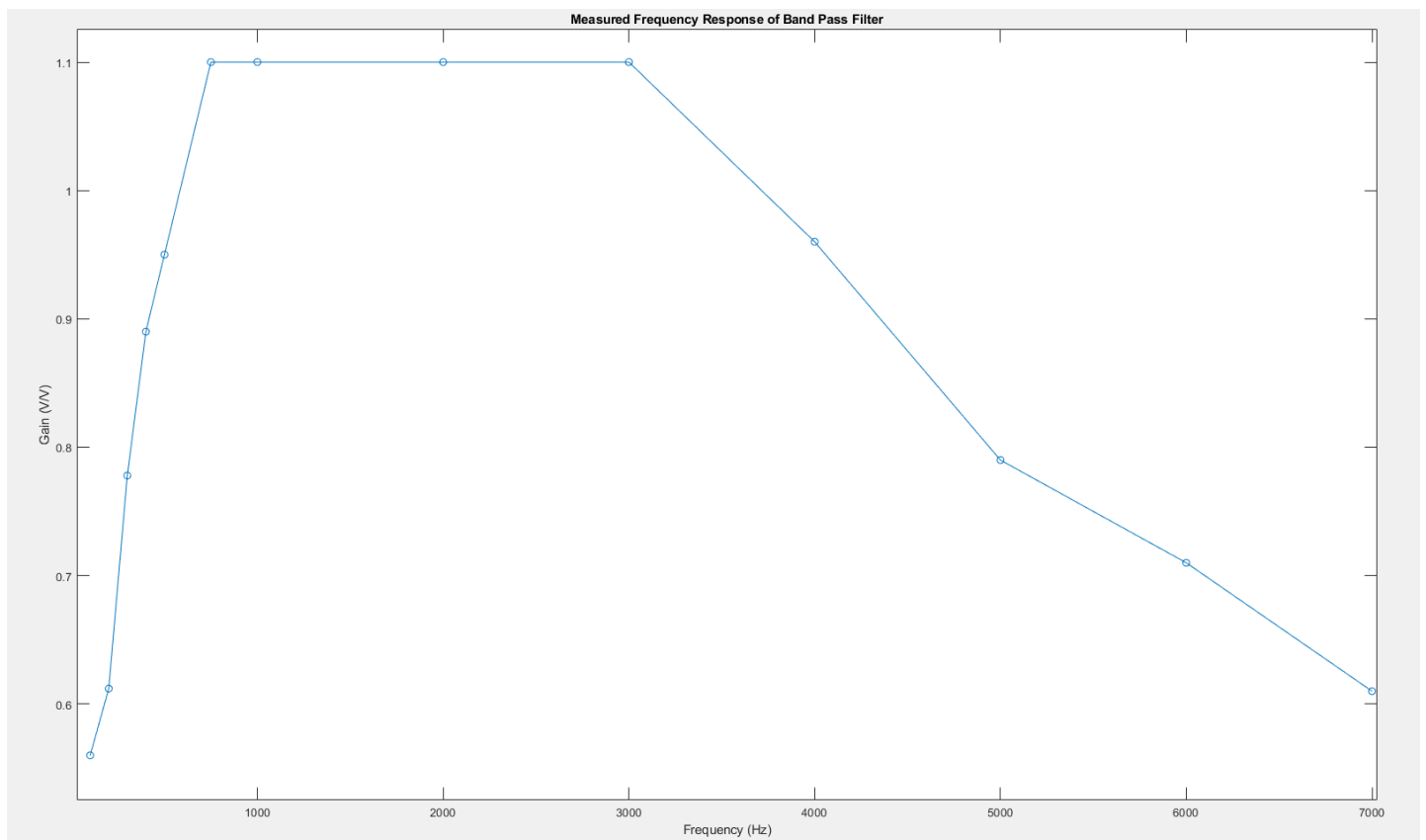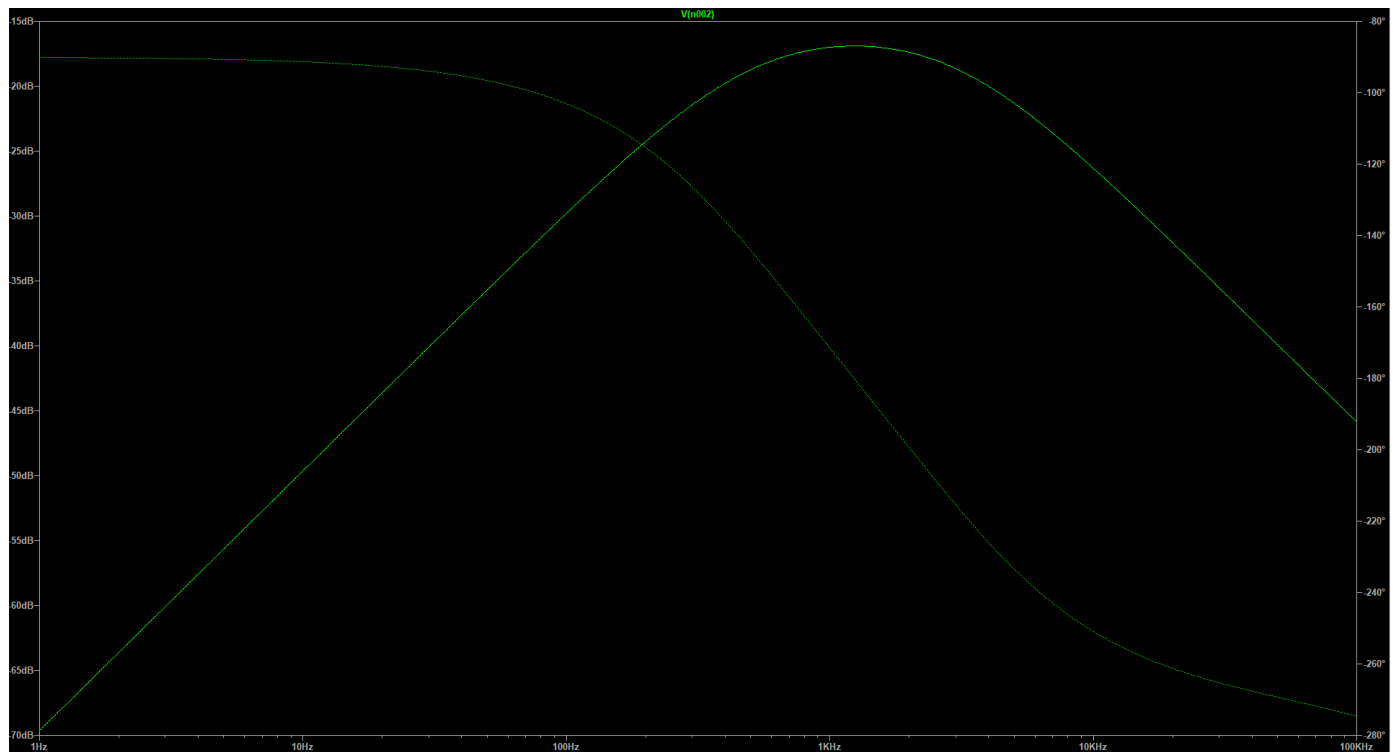

A photograph of a breadboard circuit. The breadboard is divided into four horizontal sections, each labeled 'Breadboard.com' and '050330'. The top two sections contain two integrated circuits (ICs) connected by a network of resistors and jumper wires. The bottom two sections contain another two ICs, also connected by resistors and jumper wires. The circuit is complex, with many resistors of various values and colors (brown, orange, yellow, red, green, blue) and numerous jumper wires in different colors (red, yellow, orange, black, grey, blue). The breadboard has a grid of holes with numbers 1 through 60 and letters A through J printed on it. The background is a solid blue surface.

Below is the full circuit diagram for our design.

